# **Practical 5**

Section -G2903

Name- Priyanshu

Reg. no. – 11906705


date of submission - 03/10/21

#### Aim:


To design the active filter ( band pass filter and band reject filter )

# Design and observation and result:

# For band pass filter →

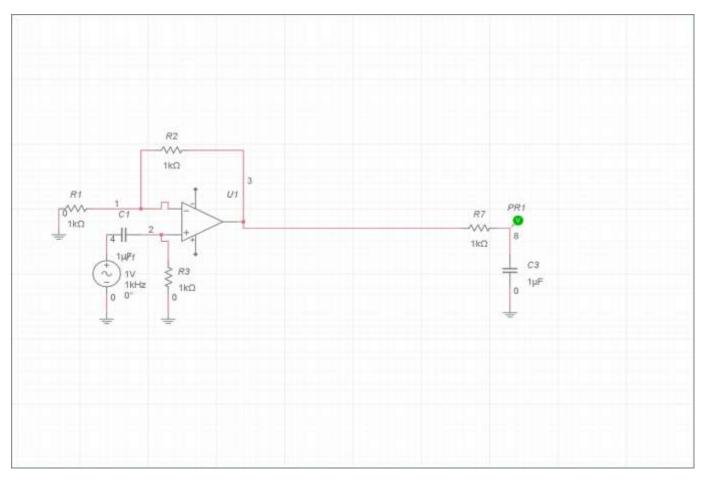

#### Excel data observation

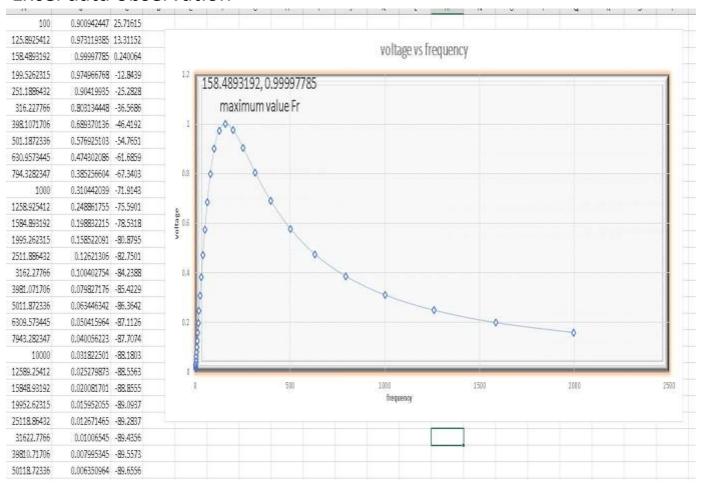

#### Calculation →

# For high pass filter =>

 $R = 1k\Omega$  and  $c = 1\mu F$ 

F\_ch= 1/2\*3.14\*1000\*10^-6=159.235hz

# For low pass filter =>

 $R=1k\Omega$  and  $c=1\mu F$ 

 $F_cl = 1/2*3.14*1000*10^-6 = 159.235hz$ 

# Now F max = (F cl\*F ch) $^{1}$ =159.235hz (theoretical value)


# Calculated from graph = 158.489hz


 $V_{max} = 999.20$  so  $V_{max} / 1.414 = 706.64$  corresponding frequency is F2 = 384.41, f1 = 65.946

So band width = f2-f1=(384.41-65.946)hz = 318.486hz

Quality factor = f\_max/bandwidth = 318.486/158.489=2.00095

# For band reject filter→

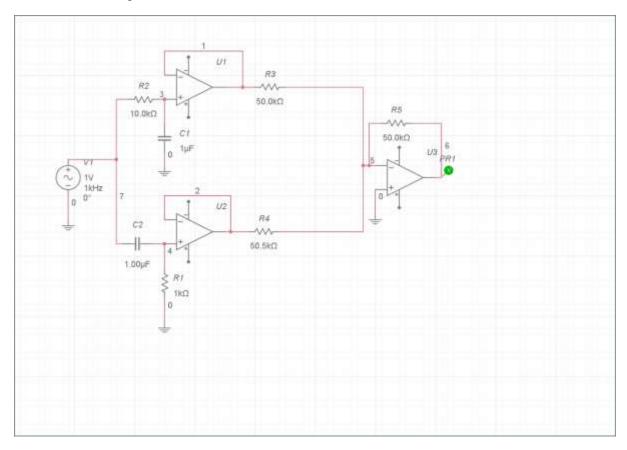

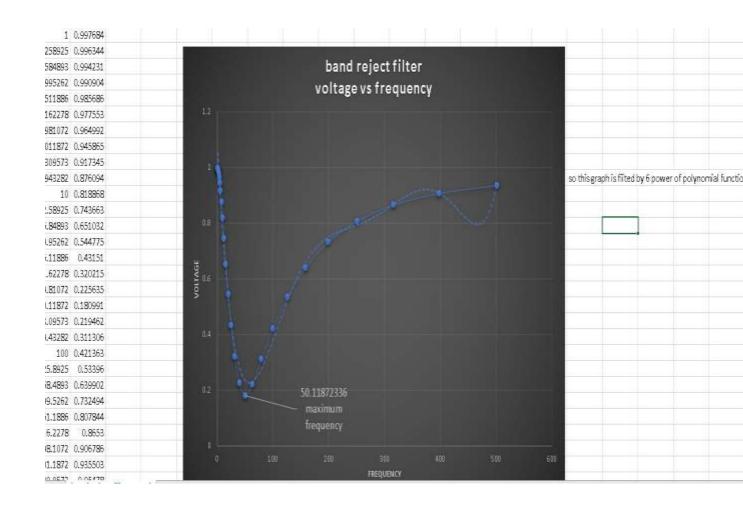

#### **Calculation**:

For high pass filter =>

 $R = 1k\Omega$  and  $c = 1\mu F$ 

F\_ch= 1/2\*3.14\*1000\*10^-6 = 159.235hz

# For low pass filter =>

 $R=10k\Omega$  and  $c=1\mu F$ 

 $F_cl = 1/2*3.14*1000*10^-6 = 15.9235hz$ 

Now F max = (F cl\*F ch)  $^{1}$ 2 =50.354hz (theoretical value)

# Calculated from graph = 50.118hz

So band width =  $f_ch-f_cl= (159.235-15.923)hz = 143.312hz$ 

Quality factor = f\_max/bandwidth = 50.118/143.312=0.3497