

Practical Submission Sheet

Term: 2020-1

Lecture Date: October 16, 2020.

Course Code: PHY249

Registration Number: 11912610

Student Name: Aayush Arya

Submission Date: October 16, 2020

Practical Number: 8

Section: G2903

Roll No: 03

Aim

To create XOR and NOT gates using NAND logic.

Concepts Learnt

Key Observations & Insights

Application Areas

Report

 


Figure 1: NAND combination for constructing the NOT (inverter) gate.

Input	Output
0	1
1	0

Table 1: Truth table for the NAND combination. It can be seen that it behaves identically to a NOT gate.

 


Figure 2: NAND logic for the XOR gate.

Input A	Input B	Output
0	0	0
0	0	1
0	1	1
0	1	0

Table 2: Truth table for the logic system in Figure 2

 


Figure 3: $f = \overline{X}.Y + \overline{X}.Z + Y.Z$